 


Q15 Design a combinational circuit that converts a 4-bit gray code to a 4-bit binary number. write the verilog dataflow model of the circuit




```

module Q_15 (G3, G2, G1, G0, B3, B2, B1, B0);
    input G3, G2, G1, G0;
    output B3, B2, B1, B0;

    assign B3 = G3;
    assign B2 = G3 ^ G2;
    assign B1 = G3 ^ G2 ^ G1;
    assign B0 = G3 ^ G2 ^ G1 ^ G0;
endmodule

```

 Q16 Construct a decoder of 5-to-32 with four 3-to-8 line decoder and a 2-to-4 line decoder. Use block diagram for the components






Q17 Use decoder and external gates, design the combinational circuit defined by the following three boolean functions

a)  $F_1 = x'y'z' + xz$

$F_2 = xy'z' + x'y$


$F_3 = x'y'z' + xy$

 

b)  $F_1 = (y' + x)z = y'z + xz$


$F_2 = y'z' + x'y + yz'$

$F_3 = (x + y)z = xz + yz$

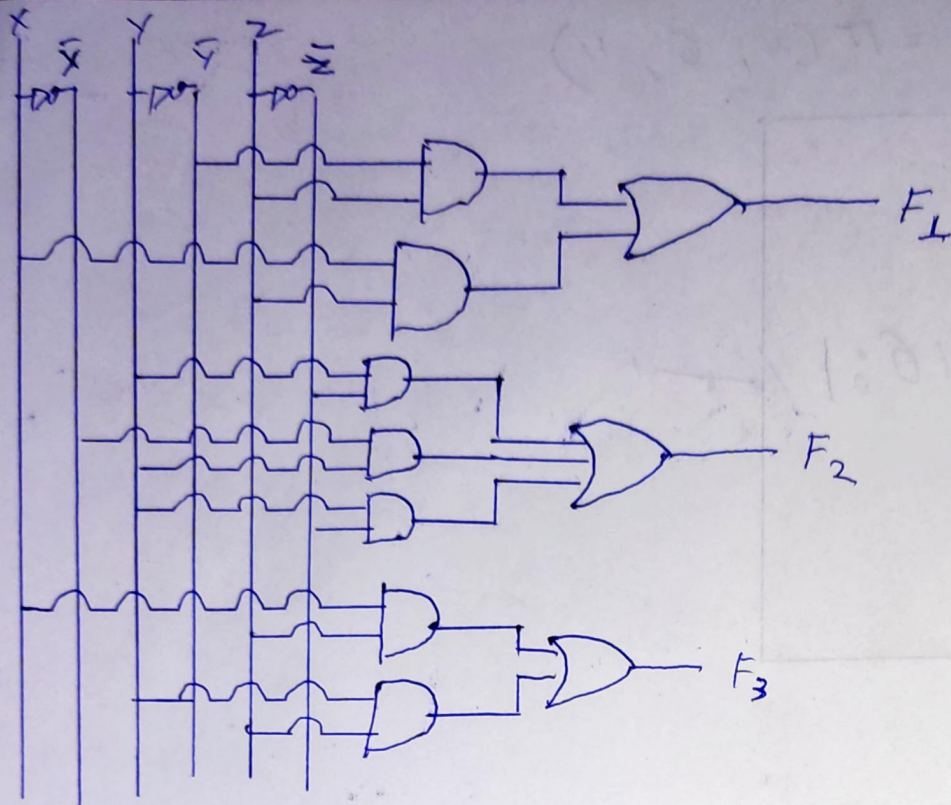


Q18 Implement the following boolean function with a multiplexer.

 (a)  $F(A, B, C, D) = \Sigma(0, 2, 5, 8, 10, 14)$






(b)  $F(A, B, C, D) = \pi(2, 6, 11)$

 

 Q19 Write HDL gate-level description of a 4-bit priority encoder circuit given below.



$$X = D_2 + D_3$$

$$Y = D_3 + D_1 D_2'$$

$$V = D_0 + D_1 + D_2 + D_3$$

module encoder-gates (Output  $x, y, v$ , ~~an~~ input  $D_0, D_1, D_2, D_3$ );

wire  $w_1, D_2\text{-not}$ ;

not( $D_2\text{-not}, D_2$ );

or( $x, D_2, D_3$ );

or( $v, D_0, D_1, x$ );

and( $w_1, D_2\text{-not}, D_1$ );

or( $y, D_3, w_1$ );

endmodule


Q20 An  $8 \times 1$  multiplexer has inputs A, B and C connected to selector input  $S_2, S_1$  and  $S_0$ . The data inputs  $I_0$  to  $I_7$  are as follows

(a)  $I_1 = I_2 = I_7 = 0$ ;

$I_3 = I_5 = 1$

$I_0 = I_4 = D$

$I_6 = D'$

 



$$(b) \quad I_1 = I_2 = 0$$

$$I_3 = I_7 = 1$$

$$I_4 = I_5 = D$$

$$I_0 = I_6 = D'$$

