

# LOGIC DESIGN

## EET-1021

CHAPTER 04

Lecture 22



# Combinational Logic

## Overview of previous lecture

- **What is Decimal adder**
- **How to construct this adder circuit**
- **What is a Magnitude Comparator circuit**


# Decoder

- A *decoder* is a combinational circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines.
- If the  $n$ -bit coded information has unused combinations, the decoder may have fewer than  $2^n$  outputs.
- The decoders presented here are called  $n$ -to- $m$ -line decoders, where  $m \leq 2^n$
- The name *decoder* is also used in conjunction with other code converters, such as a BCD-to-seven-segment decoder.

## Truth Table of a Three-to-Eight-Line Decoder

For each possible input combination, there are seven outputs that are equal to 0 and only one that is equal to 1. The output whose value is equal to 1 represents the minterm equivalent of the binary number currently available in the input lines.

Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>	<i>D</i> <sub>4</sub>	<i>D</i> <sub>5</sub>	<i>D</i> <sub>6</sub>	<i>D</i> <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 


**Three-to-eight-line decoder**

A decoders include one or more *enable inputs to control the circuit operation*. A two-to-four-line decoder with an enable input is constructed with NAND gates.

The circuit operates with complemented outputs and a complement enable input. The decoder is enabled when *E* is equal to 0 (i.e., active-low enable).

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	1

Truth table

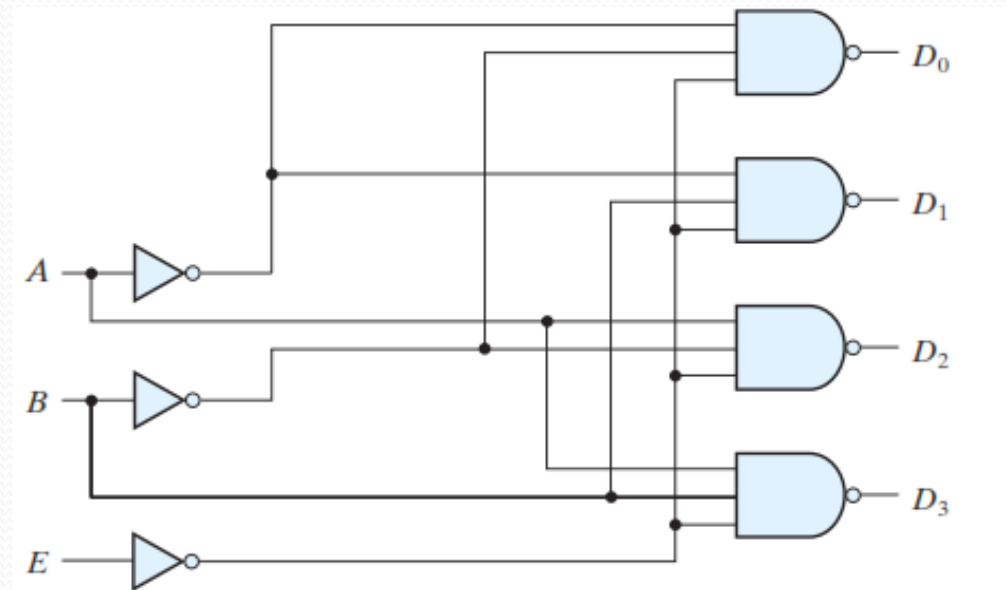

Logic Diagram

- A decoder with enable input can function as a *demultiplexer*—*a circuit that receives* information from a single line and directs it to one of  $2^n$  possible output lines. The selection of a specific output is controlled by the bit combination of *n selection lines*.
- The decoder above shown can function as a one-to-four-line demultiplexer when *E* is taken as a data input line and *A* and *B* are taken as the selection inputs.
- The single input variable *E* has a path to all four outputs, but the input information is directed to only one of the output lines, as specified by the binary combination of the two selection lines *A* and *B*.
- As decoder and demultiplexer operations are obtained from the same circuit, a decoder with an enable input is referred to as a *decoder – demultiplexer*.



## HDL for 2 to 4 line Decoder:

// Gate-level description of two-to-four-line decoder

```
module decoder_2x4_gates (D, A, B, enable);
```

```
  output [0:3] D;
```

```
  input  A, B, enable;
```

```
  wire  A_not, B_not, enable_not;
```

```
  not
```

```
    G1 (A_not, A),
```

```
    G2 (B_not, B),
```

```
    G3 (enable_not, enable);
```

```
  nand
```


```
    G4 (D[0], A_not, B_not, enable_not),
```

```
    G5 (D[1], A_not, B, enable_not),
```

```
    G6 (D[2], A, B_not, enable_not),
```

```
    G7 (D[3], A, B, enable_not);
```

```
endmodule
```

 

# Dataflow Modeling

```
//Dataflow description of a 2-to-4-line decoder
module decoder_df (A,B,E,D);
    input A,B,E;
    output [0:3] D;
    assign D[0] = ~(~A & ~B & ~E),
           D[1] = ~(~A & B & ~E),
           D[2] = ~(A & ~B & ~E),
           D[3] = ~(A & B & ~E);

endmodule
```


A 2-to-1 line multiplexer with data inputs A and B, select input S, and output Y is described with the continuous assignment

```
assign Y = (A & S) | (B & ~S)
```
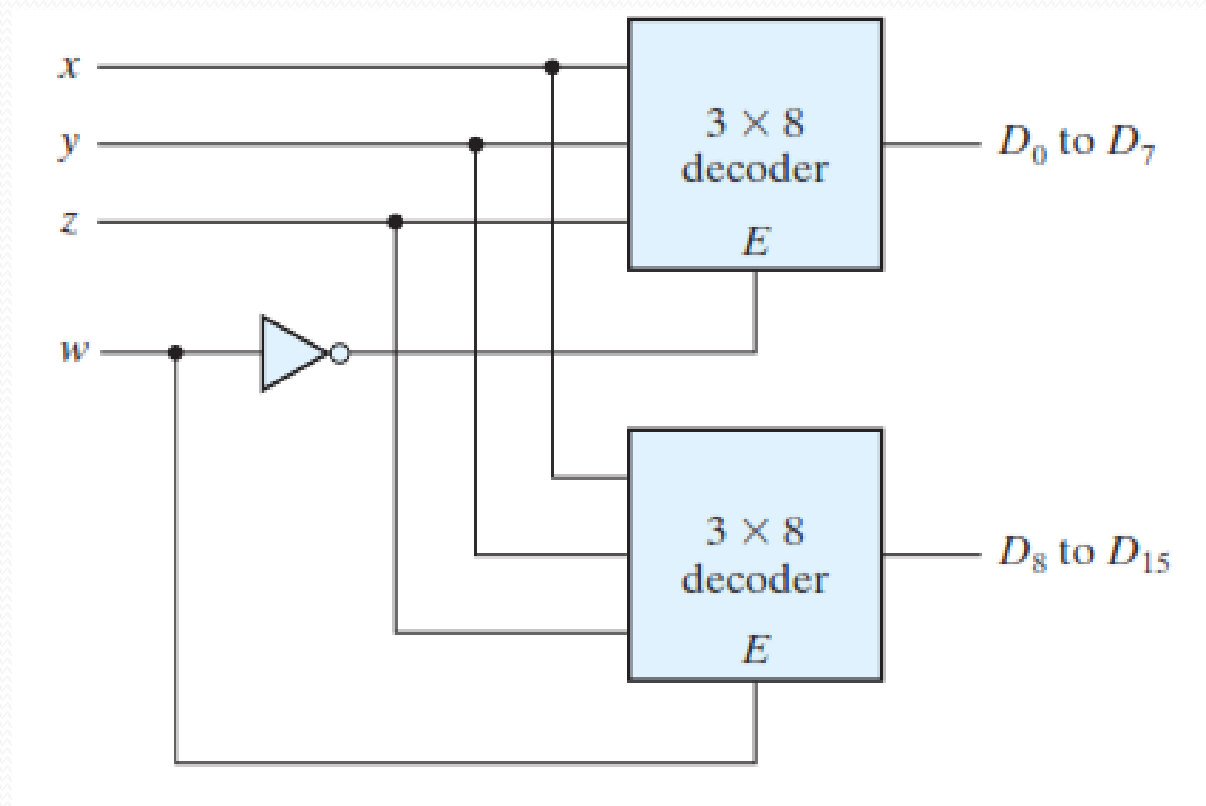
# Behavioral Model

```
module decoder(sel,en,y);  
    input [1:0] sel;  
    input en;  
    output [3:0] y;  
  
    reg y;  
  
    always @(sel, en)  
    begin // required if multiple sequential statements  
        if (en == 0)  
            y = 4'b1111;  
        else  
            if (sel == 2'b00)  
                y = 4'b1110;  
            else if (sel == 2'b01)  
                y = 4'b1101;  
            else if (sel == 2'b10)  
                y = 4'b1011;  
            else  
                y = 4'b0111;  
        end  
    end  
endmodule
```

Decoders with enable inputs can be connected together to form a larger decoder circuit




$4 \times 16$  decoder constructed with two  $3 \times 8$  decoders

# Combinational Logic Implementation

Since any Boolean function can be expressed in sum-of-minterms form, a decoder that generates the minterms of the function, together with an external OR gate that forms their logical sum, provides a hardware implementation of the function. In this way, any combinational circuit with  $n$  inputs and  $m$  outputs can be implemented with an  $n$ -to- $2^n$ -line decoder and  $m$  OR gates.

$$S(x, y, z) = \Sigma(1, 2, 4, 7)$$

$$C(x, y, z) = \Sigma(3, 5, 6, 7)$$

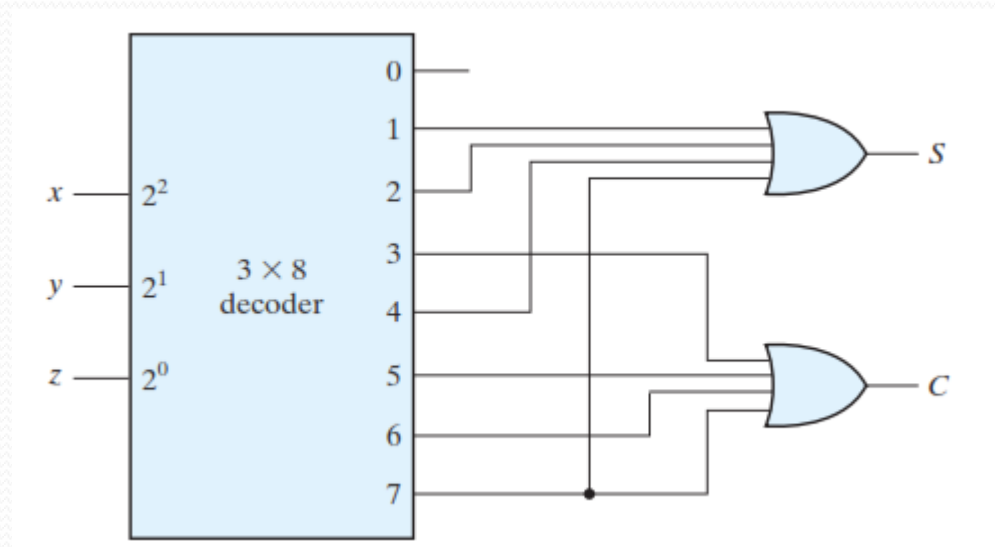

Implementation of a full adder with a decoder

# Encoder

- An encoder is a digital circuit that performs the inverse operation of a decoder. An encoder has  $2^n$ (or fewer) **input lines** and  **$n$  output lines**. *The output lines, as an aggregate, generate the binary code corresponding to the input value.*
- Let us consider an example of an encoder i.e the **octal-to-binary encoder**

It has eight inputs (one for each of the octal digits) and three outputs that generate the corresponding binary number. It is assumed that only one input has a value of 1 at any given time.

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

**Truth Table of an Octal-to-Binary Encoder**

The encoder can be implemented with OR gates whose inputs are determined directly from the truth table. These conditions can be expressed by the following Boolean output functions:

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

The encoder can be implemented with three OR gates.



# Limitation

- The encoder defined above has the limitation that only one input can be active at any given time. If two inputs are active simultaneously, the output produces an undefined combination.
- To resolve this ambiguity, encoder circuits must establish an input priority to ensure that only one input is encoded.
- Another ambiguity in the octal-to-binary encoder is that an output with all 0's is generated when all the inputs are 0; but this output is the same as when  $D$  is equal to 1. The discrepancy can be resolved by providing one more output to indicate whether at least one input is equal to 1.

# Priority Encoder

- A priority encoder is an encoder circuit that includes the priority function.
- The truth table of a four-input priority encoder is given below.

## Truth Table of a Priority Encoder

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

In addition to the two outputs  $x$  and  $y$ , the circuit has a third output designated by  $V$ ; this is a valid bit indicator that is set to 1 when one or more inputs are equal to 1. Note that whereas X's in output columns represent don't-care conditions, the X's in the input columns are useful for representing a truth table in condensed form

$D_0D_1$ \ $D_2D_3$		$D_2$			
		00	01	11	10
$D_0$	00	$m_0$ X	$m_1$ 1	$m_3$ 1	$m_2$ 1
	01	$m_4$	$m_5$ 1	$m_7$ 1	$m_6$ 1
	11	$m_{12}$	$m_{13}$ 1	$m_{15}$ 1	$m_{14}$ 1
	10	$m_8$	$m_9$ 1	$m_{11}$ 1	$m_{10}$ X

$x = D_2 + D_3$


$D_0D_1$ \ $D_2D_3$		$D_2$			
		00	01	11	10
$D_0$	00	$m_0$ X	$m_1$ 1	$m_3$ 1	$m_2$
	01	$m_4$ 1	$m_5$ 1	$m_7$ 1	$m_6$
	11	$m_{12}$ 1	$m_{13}$ 1	$m_{15}$ 1	$m_{14}$
	10	$m_8$	$m_9$ 1	$m_{11}$ 1	$m_{10}$

$y = D_3 + D_1 D'_2$

$$x = D_2 + D_3$$

$$y = D_3 + D_1 D'_2$$


$$V = D_0 + D_1 + D_2 + D_3$$

 

**Four-input priority encoder**


# HDL for Priority Encoder

```
module PriorityEncoder_4Bit(  
    input [0:3] D,  
    output [1:0] Y,  
    output V  
);  
    reg [1:0] Y;  
    reg V;  
    always @(D)  
    begin  
        Y[1] <= D[2] | D[3];  
        Y[0] <= D[3] | D[1] & ~D[2];  
        V = D[0] | D[1] | D[2] | D[3];  
    end  
endmodule
```

 

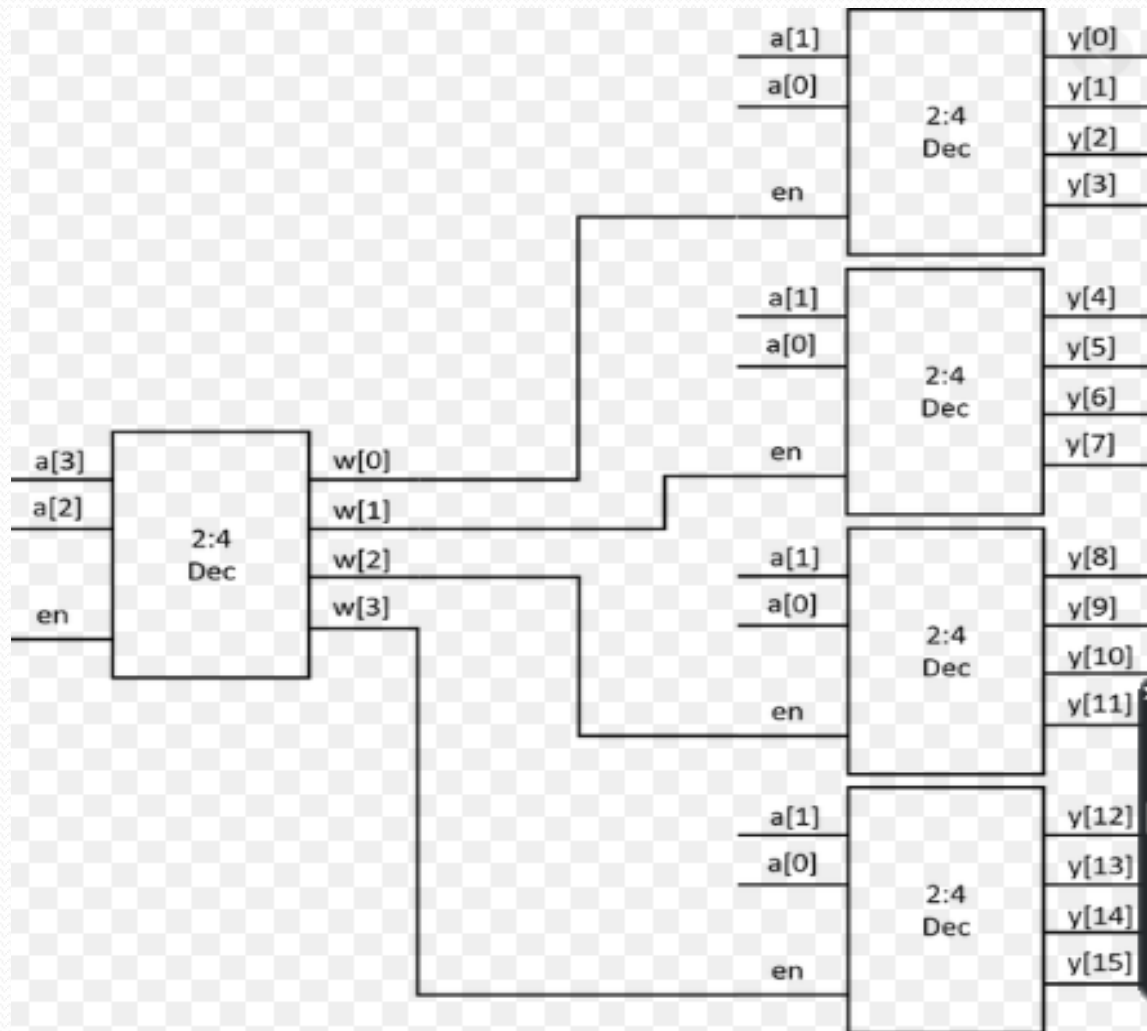
# Example

Construct a 4-to-16-line decoder with five 2-to-4-line decoders with enable.



 Construct a 5-to-32-line decoder with four 3-to-8-line decoders with enable and a 2-to-4-line decoder. Use block diagrams for the components.







THANK YOU