

DIGITAL LOGIC DESIGN LAB (EET1211)

LAB V: DESIGN AND TEST VARIOUS CODE CONVERTER CIRCUITS

Siksha 'O' Anusandhan Deemed to be University, Bhubaneswar

Branch:			Section:
S. No.	Name	Registration No.	Signature

Marks: ____/10

Remarks:

Teacher's Signature

I. OBJECTIVE:

1. Design a combinational circuit with four input lines that represent a decimal digit in BCD and four output lines that generate the 9's complement of the input digit.
2. Design a combinational circuit with four inputs and four outputs that converts a 4bit binary number into the equivalent 4bit Gray code.
3. Design a combinational circuit that accepts a 2-bit number and generates an output binary number equal to the square of the input number.

II. PRE-LAB

For Obj. 1:

- a. Write the truth table for the circuit.
- b. Derive the Minimized Boolean expression for each output of the circuit.
- c. Draw the logic diagram for the circuit.
- d. Write HDL code.

For Obj. 2:

- a. Write the truth table for the circuit.
- b. Derive the Minimized Boolean expression for each output of the circuit.
- c. Draw the logic diagram for the circuit.
- d. Write HDL code.

For Obj. 3:

- a. Write the truth table for the circuit.
- b. Derive the Minimized Boolean expression for each output of the circuit.
- c. Draw the logic diagram for the circuit.
- d. Write HDL code.

III. LAB:

Components Required:

<u>S. No</u>	<u>Name of the Component</u>	<u>Specification</u>	<u>Quantity</u>
--------------	------------------------------	----------------------	-----------------

HDL Program:

Observation:

Conclusion:

IV. POST LAB:

1. Design a BCD to excess-3 code converter using the unused combinations of the code as don't-care conditions.
2. What is the advantage of Gray code?
3. Draw the logic circuit that converts a 4 bit Gray code to binary code.