

DIGITAL LOGIC DESIGN LAB (EET1211)

LAB II: Examine & Analyze Advantages of Gate Level Minimization for Boolean Function

Siksha 'O' Anusandhan Deemed to be University, Bhubaneswar

Branch:			Section:
S. No.	Name	Registration No.	Signature

Marks: ____/10

Remarks:

Teacher's Signature

I. OBJECTIVE:

1. Construct a circuit using basic gates that implements the Boolean function given below and record the output for all sets of input.

$$F = AB + AB'C$$

- a. Simplify the Boolean function using minimization technique.
 - b. Construct the circuit for the simplified expression using basic gates & verify the truth table.
2. Simplify the following Boolean functions to minimum number of literals and design the circuit using basic gates.

a) $F = XY + X'Z + YZ$

b) $F = (X'Y' + Z)' + Z + XY + WZ$

3. Consider two Boolean functions in sum-of-min terms form:

$$F1(A, B, C, D) = (0, 1, 2, 3, 4, 6, 8, 9, 10, 11)$$

$$F2(A, B, C, D) = (3, 5, 7, 8, 10, 11, 13, 15)$$

- a. Implement both the functions using a minimum number of NAND ICs & verify the truth tables.
- b. Implement both the functions using minimum number of basic gates.

II. PRE-LAB

For Obj. 1:

- a. Draw the circuit diagram.
- b. Obtain the truth table for F as function of 3 inputs.
- c. Simplify the Boolean function using Boolean algebra rules & verify the correctness of the simplified expression using truth table.
- d. Draw the logic diagram of simplified Boolean expression

For Obj. 2:

- a) Draw the circuit diagram and obtain the truth table for all input combinations.
- b) Simplify the functions.
- c) Draw the circuit & write truth table for minimized functions.

For Obj. 3:

- a) Simplify the given expressions using k-map.
- b) Obtain a composite logic diagram with four inputs, A, B, C and D, and two outputs, F1, and F2. Obtain truth tables for both the functions.

III. LAB:

Components Required:

<u>S. No</u>	<u>Name of the Component</u>	<u>Specification</u>	<u>Quantity</u>
--------------	------------------------------	----------------------	-----------------

Observation:

Conclusion:

IV. POST LAB:

1. What is the advantage of Boolean laws?
2. What is a K-map? What are its advantages and disadvantages?
3. What ways can Boolean expressions be represented?
4. Implement two input Ex-NOR gate using minimum number of two input NOR gates.