

LOGIC DESIGN

EET-1021

CHAPTER 04
Lecture 23




Combinational Logic

Overview of previous lecture


- **What is Decoder**
- **What is Encoder**
- **Limitation of Encoder**
- **Priority Encoder**

Multiplexers

- A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line. The selection of a particular input line is controlled by a set of selection lines. Normally, there are 2^n input lines and n selection lines whose bit combinations determine which input is selected.
- In general, a 2^n -to-1-line multiplexer is constructed from an n -to- 2^n decoder by adding 2^n input lines to it, one to each AND gate. The outputs of the AND gates are applied to a single OR gate.

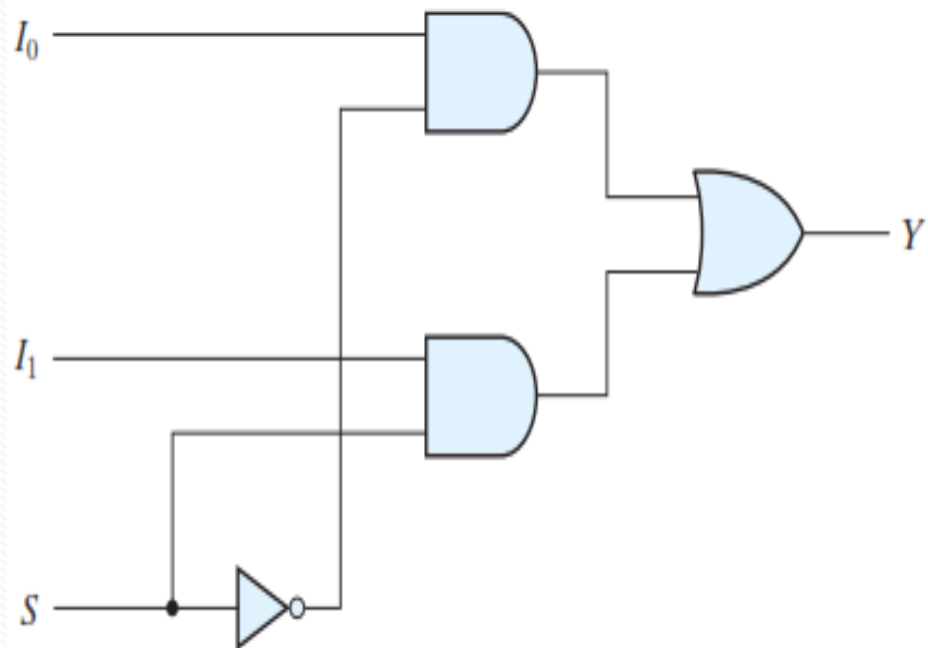


(a) Logic diagram

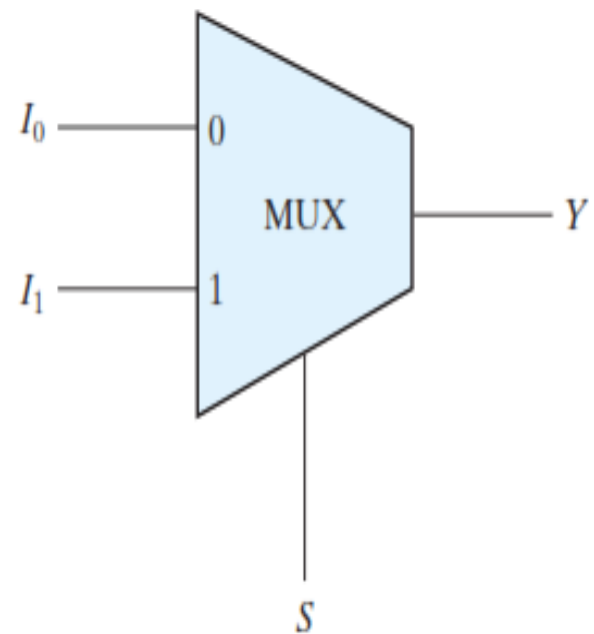

(b) Block diagram

Two-to-one-line multiplexer

 

(a) Logic diagram

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table


Four-to-one-line multiplexer

Boolean Function Implementation

$$F(x, y, z) = \Sigma(1, 2, 6, 7)$$

x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

 


(b) Multiplexer implementation

As a second example, consider the implementation of the Boolean function

$$F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$


<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

 


Implementing a four-input function with a multiplexer

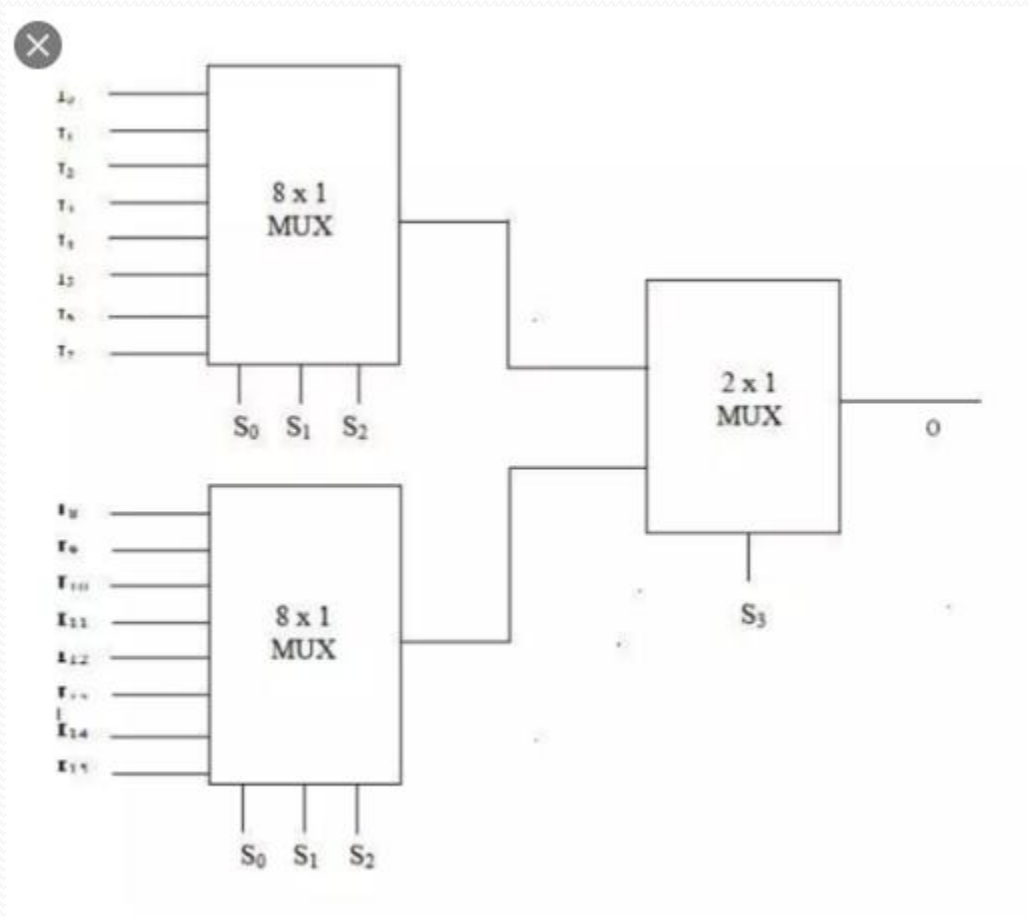Example

Construct a 16×1 multiplexer with two 8×1 and one 2×1 multiplexers.



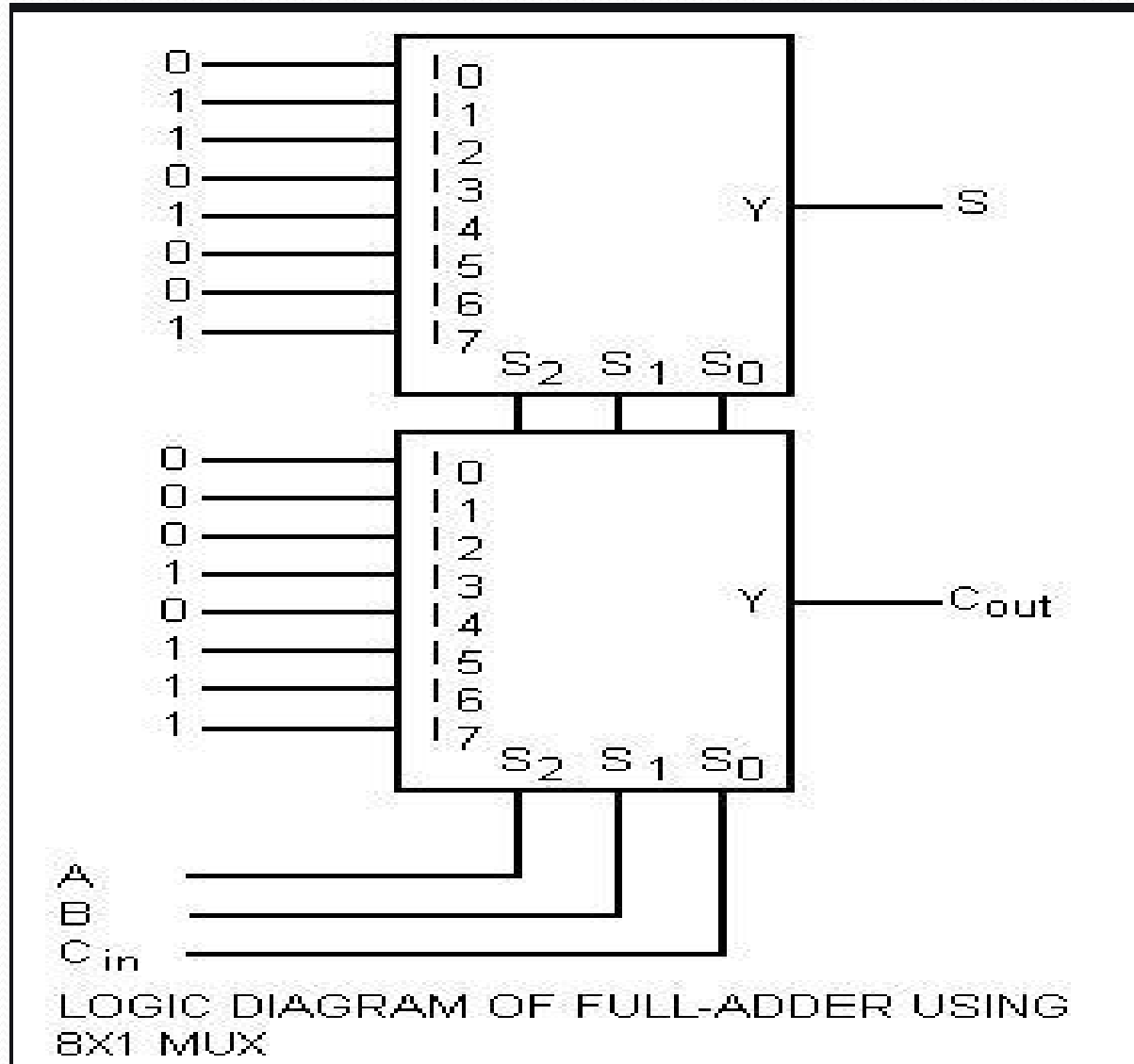
Implement a full adder with two 8×1 multiplexers.



Implement the given Boolean function by using 8×1 multiplexer.


$$F(A,B,C,D) = \Sigma(0,1,3,4,8,9,15)$$

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
A'	①	①	2	③	④	5	6	7
A	⑧	⑨	10	11	12	13	14	⑮
	1	1	0	A'	A'	0	0	A

 

Implement XOR gate by using 2×1 Multiplier

Inputs		Output
A	B	OUT
0	0	0
0	1	1
1	0	1
1	1	0

 



THANK YOU