

DIGITAL LOGIC DESIGN LAB (EET1211)

LAB VI: DESIGN OF MAGNITUDE COMPARATOR, DECODER, ENCODER AND MULTIPLEXER CIRCUIT

Siksha 'O' Anusandhan Deemed to be University, Bhubaneswar

Branch: CSE			Section: M
S. No.	Name	Registration No.	Signature
1.	BISWARANTAN SAHOO	2141019075	Biswarantan Sahoo

Marks: ____/10

Remarks:

Teacher's Signature

I. OBJECTIVE:

1. Design a combinational circuit that compares two 4-bit numbers to check if they are equal. The circuit output is equal to 1 if the two numbers are equal and 0 otherwise.
2. Design a 2 X 1 Multiplexer that will select the binary information from one of the two input lines and direct it to a single output line based on the value of a selection line.
3. Design a 4 bit priority encoder with inputs D_3 (MSB), D_2 , D_1 and D_0 (LSB) and outputs X, Y and V. The priority assigned to inputs is $D_3 > D_2 > D_1 > D_0$. The output V shows a value 1 when one or more inputs are equal to one. If all inputs are 0, V is equal to 0. When V=0, then other two outputs are not inspected and are specified as don't care conditions.
4. Design a full adder using 3 to 8 line decoder and external OR gates.

II. PRE-LAB

For Obj. 1:

- a. Write the truth table for the circuit.
- b. Derive the Minimized Boolean expression for the output of the circuit.
- c. Draw the logic diagram for the circuit.
- d. Write HDL code.

For Obj. 2:

- a. Write the truth table for the circuit.
- b. Derive the Minimized Boolean expression for the output of the circuit.
- c. Draw the logic diagram for the circuit.
- d. Write HDL code.

For Obj. 3:

- a. Write the truth table for the circuit.
- b. Derive the Minimized Boolean expression for each output of the circuit.
- c. Draw the logic diagram for the circuit.
- d. Write HDL code.

For Obj. 4:

- a. Write the truth table for the circuit.
- b. Derive the Boolean expression for each output of the circuit.
- c. Draw the logic diagram for the circuit.
- d. Write HDL code.

OBJECTIVE - 1

$A \rightarrow A_3 \ A_2 \ A_1 \ A_0$

$B \rightarrow B_3 \ B_2 \ B_1 \ B_0$

$$(A=B) \rightarrow (A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) (A_0 \odot B_0)$$


a)

A_3	A_2	A_1	A_0	B_3	B_2	B_1	B_0	$F (A=B)$
1	0	0	1	0	0	1	1	0
1	1	0	0	1	1	0	0	1
0	0	1	0	0	0	1	0	1
0	0	0	1	0	1	1	0	0

b) Minimized Eqⁿ

$$(A=B) \Rightarrow (A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) (A_0 \odot B_0)$$

c)

 

d) HDL Code

```
module obj1 (A3, A2, A1, A0, B3, B2, B1, B0, F);
```

```
input A3, A2, A1, A0, B3, B2, B1, B0;
```

```
output F;
```

```
assign F = (!(A3 ^ B3)) & (!(A2 ^ B2)) & (!(A1 ^ B1)) & (!(A0 ^ B0));
```

```
end module
```


OBJECTIVE-2

a) $Y = SA_1 + \bar{S}A_0$


S	A ₀	A ₁	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

b)

S \ A ₀ A ₁	00	01	11	10
0			1	1
1		1	1	

$Y = SA_1 + \bar{S}A_0$

c)

 

d) HDL Code

```

module obj2(S, A0, A1, Y);
input S, A0, A1;
output Y;
assign Y = (S & A1) || (~S & A0);
end module
    
```

OBJECTIVE-3

a)

D ₃	D ₂	D ₁	D ₀	X	Y	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

b)

D ₃ D ₂ \ D ₁ D ₀	00	01	11	10
00	X	0	0	0
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$X = D_3 + D_2$


D ₃ D ₂ \ D ₁ D ₀	00	01	11	10
00			1	1
01				
11	1	1	1	1
10	1	1	1	1

$Y = D_3 + D_1\bar{D}_2$

D ₃ D ₂ \ D ₁ D ₀	00	01	11	10
00	0	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$V = D_3 + D_2 + D_1 + D_0$

7

 

d)

```

module obj3(D0, D1, D2, D3, X, Y, V);
  input D0, D1, D2, D3;
  output X, Y, V;

  assign X = D2 || D3;
  assign Y = (D1 & ~D2) || D3;
  assign V = D0 || D1 || D2 || D3;
end module
  
```


OBJECTIVE-4

a)

A	B	C	Sum	Carry	X	Y	Z	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	1	0	0	0	1	0	0	0	0	0	0	1	0
0	1	0	1	0	0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	1	0	1	1	0	0	0	0	1	0	0	0
1	0	0	1	0	1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0

b) $Sum = D_1 + D_2 + D_4 + D_7$

$Carry = D_3 + D_5 + D_6 + D_7$

 

```

d) module alj4(x, y, z, sum, carry);
    input x, y, z;
    output sum, carry;
    assign sum = (~x & ~y & z) | (~x & y & ~z) | (x & ~y & ~z) | (x & y & z);
    assign carry = (~x & y & z) | (x & ~y & ~z) | (x & y & ~z) | (x & y & z);
endmodule

```