

For Objective-1:

2)

	A	B	C	D	F
	0	0	0	0	0
	0	0	0	1	0
	0	0	1	0	0
	0	0	1	1	0
	0	1	0	0	0
	0	1	0	1	1
	0	1	1	0	1
	0	1	1	1	1
	1	0	0	0	1
	1	0	0	1	1
	1	0	1	0	1
	1	0	1	1	1
	1	1	0	0	0
	1	1	0	1	0
	1	1	1	0	0
	1	1	1	1	0


3)

AB	$CD$	$CD'$	$C'D$	$C'D'$
$A'B'$				
$A'B$		1	1	1
$AB$				
$AB'$	1	1	1	1

Simplified expression:

$$AB' + A'B + AB$$

c)

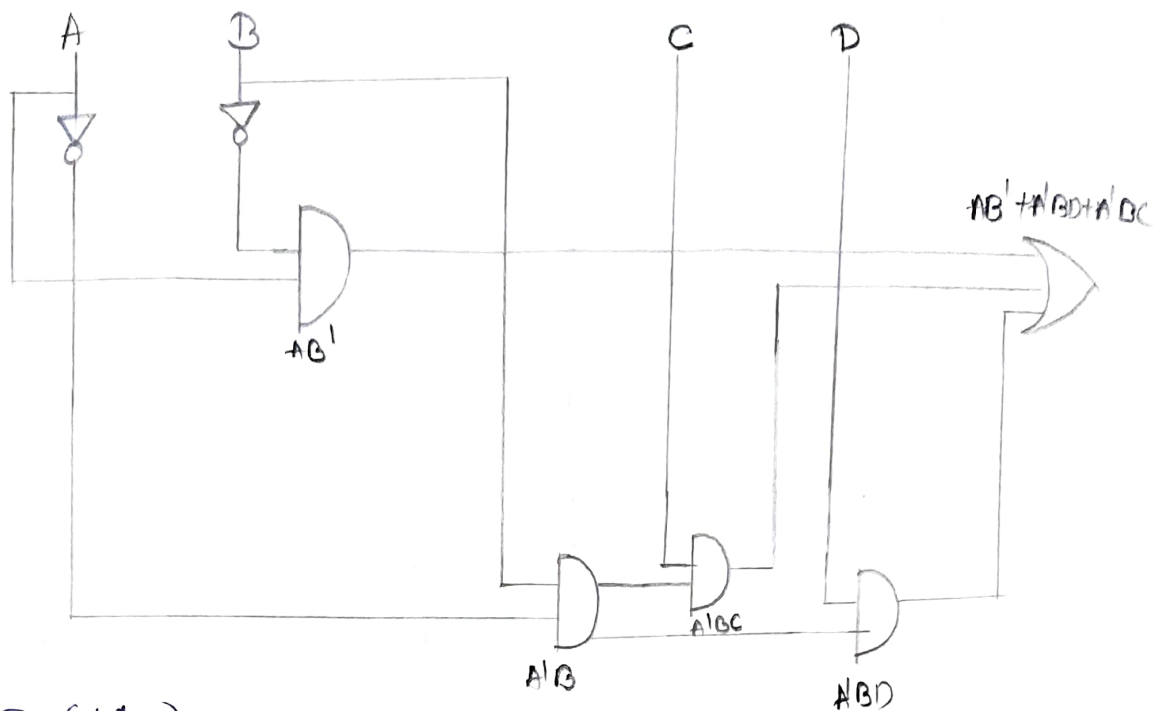

For (obj-2)


a)

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

b)

	BC	B'C	BC'	B'C'
A			1	
A'		1	1	1

Expression:-  $AB + AC + BC$

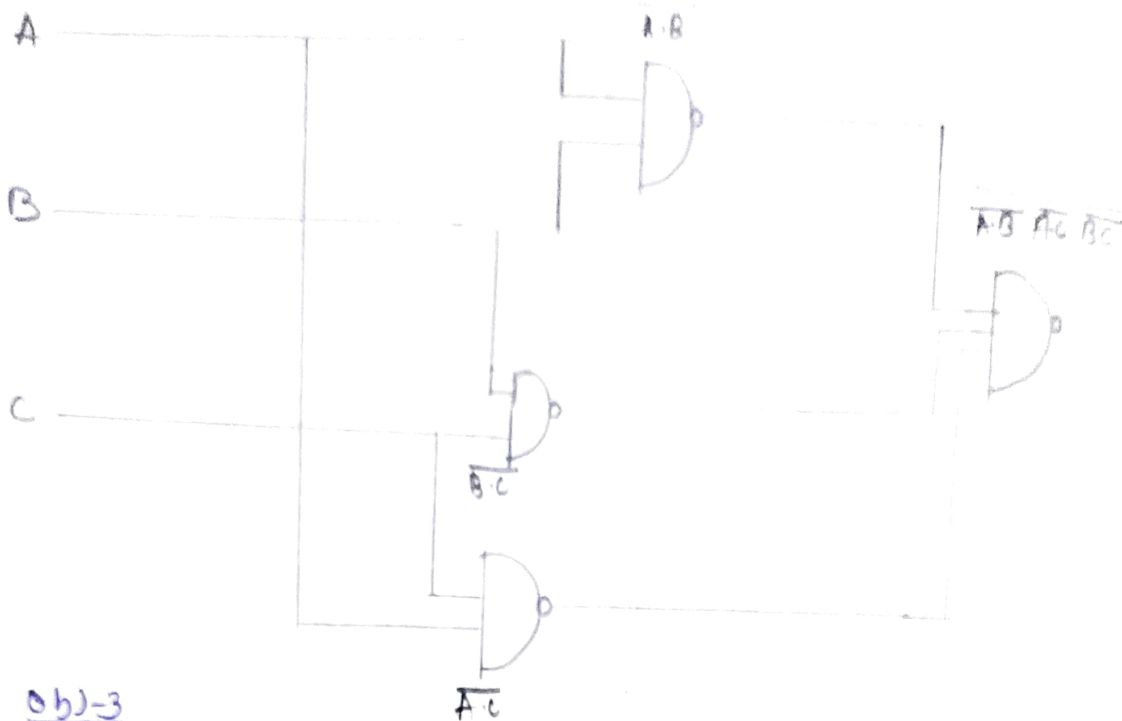

Obj-3

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

b)  $F(A, B, C, D) = \sum (1, 2, 4, 7, 8, 11, 13, 14)$


AB \ CD	00	01	10	11
00	0	1	0	1
01	1	0	1	0
10	0	1	0	1
11	1	0	1	0

$$\begin{aligned}
 &= A'B'C'D + A'B'CD' + A'BC'D + A'BCD' + AB'C'D + AB'CD' + AB'C'D' + AB'CD \\
 &= A'B'(C'D + C'D') + A'B(C'D' + CD) + AB(C'D + CD') + AB'(C'D' + CD) \\
 &= A'B'(C \oplus D) + A'B(C \odot D) + AB(C \oplus D) + AB'(C \odot D) \\
 &= A'B'(C \oplus D) + AB(C \oplus D) + A'B(C \odot D) + AB'(C \odot D) \\
 &= (C \oplus D)(A'B' + AB) + (C \odot D)(A'B + AB') \\
 &= (C \oplus D)(A \oplus B) + (C \odot D)(A \oplus B)
 \end{aligned}$$

Considering  $A \oplus B$  as  $x$  and  $C \oplus D$  as  $y$

So the expression will be  $yx' + xy' = x \oplus y$

$$= (A \oplus B) \oplus (C \oplus D)$$

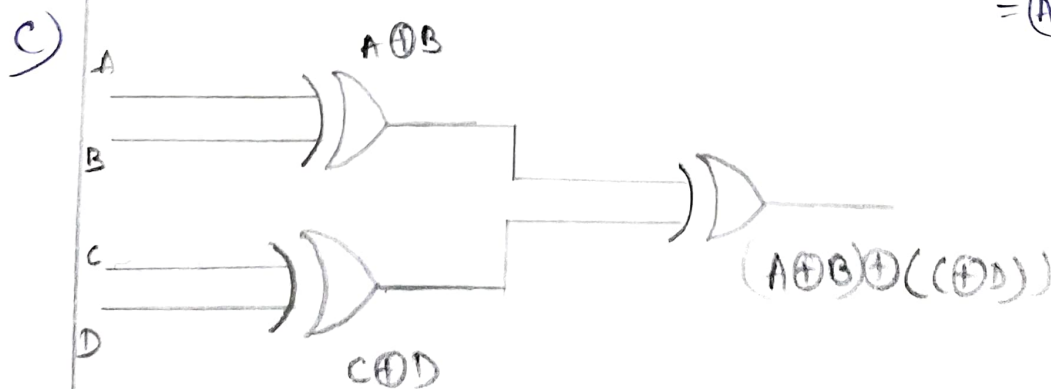

053-4


A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0
1	1	1	1	1

$$F(A, B, C, D) = \sum (0, 5, 10, 15)$$

AB \ CD	00	01	10	11
A'B'	1			
A'B		1		
AB			1	
AB'				1

$$\begin{aligned}
 F &= A'B'C'D' + A'B'CD + ABC'D + AB'CD \\
 &= A'C'(B'D' + BD) + AC(B'D + B'D) \\
 &= A'C'(B \oplus D)' + AC(B \oplus D) \\
 &= (B \oplus D)' (A'C' + AC) \\
 &= (A \oplus C)' (B \oplus D)
 \end{aligned}$$

c)

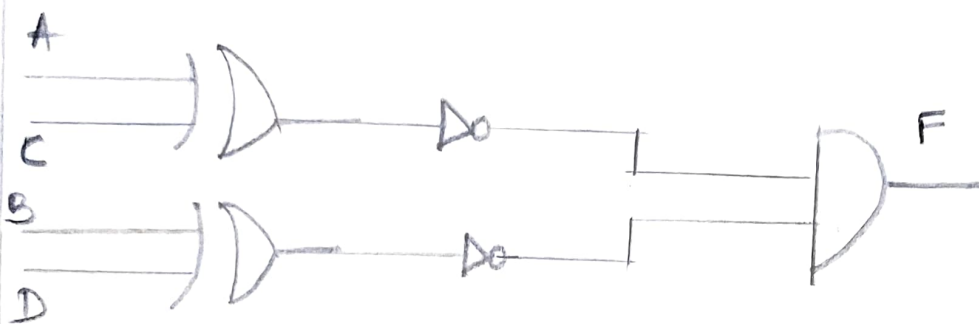

## Components required

### Quantity

IC 7408	- Quad 2 input AND gate	- 1
IC 7432	- Quad 2 input OR gate	- 1
IC 7404	- Hex Inverter NOT gate	- 1
IC 7400	- Quad 2 input NAND gate	- 1
IC 7410	- <del>Quad</del> 3 input NAND gate	- 1
IC 7486	- Quad 2 input XOR gate	- 1

Connecting wires

## Observation

A	B	C	D	F	
0	0	0	0	0	
0	0	0	1	0	
0	0	1	0	0	
0	0	1	1	0	
0	1	0	0	0	
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	1	
1	0	0	1	1	
1	0	1	0	1	
1	0	1	1	1	
1	1	0	0	0	
1	1	0	1	0	
1	1	1	0	0	
1	1	1	1	0	

ob)-2

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

ob)-3

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0



Obj-y

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Conclusion

1. From the observation it can be concluded that for getting the output as per the instruction the Combinational circuit leads to the function i.e  $AB' + A'BD + A'BC$ .

2. 3 input majority circuit leads to the function  $AB + AC + BC$
3. The even parity bit from 4 message bits leads to the function  $A \oplus B \oplus C \oplus D$
4. The equality condition leads to the XNOR function  $(A \oplus C)' (B \oplus D)'$

### Post Lab

1. A majority logic is a digital logic circuit whose output is equal to 1 if the majority of the inputs are 1's i.e. The output is '0' otherwise.
2. Take XOR of it with high input i.e. 1
3. The function of a magnitude comparator circuit is to determine whether one no. is greater than, less than or equal to the other no.