

DIGITAL LOGIC

LECTURE-21



◦ Decimal Adder

- An adder for a computer that employ arithmetic circuits that accept coded decimal numbers and present results in the same code.
- A decimal adder requires a minimum of nine inputs and five outputs, since four bits are required to code each decimal digit and the circuit must have an input and output carry.
- There is a wide variety of possible decimal adder circuits, depending upon the code used to represent the decimal digits.
- Here we examine a decimal adder for the BCD code.



BCD Adder

- Consider the arithmetic addition of two decimal digits in BCD, together with an input carry from a previous stage.
- Since each input digit does not exceed 9, the output sum cannot be greater than $9 + 9 + 1 = 19$, the 1 in the sum being an input carry.
- Suppose we apply two BCD digits to a four-bit binary adder.



Derivation of BCD Adder


<i>K</i>	Binary Sum				BCD Sum					Decimal
	<i>Z</i> ₈	<i>Z</i> ₄	<i>Z</i> ₂	<i>Z</i> ₁	<i>C</i>	<i>S</i> ₈	<i>S</i> ₄	<i>S</i> ₂	<i>S</i> ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19



- The logic circuit that detects the necessary correction can be derived from the entries in the table. It is obvious that a correction is needed when the binary sum has an output carry $K = 1$.
- The condition for a correction and an output carry can be expressed by the Boolean function

$$C = K + Z_8Z_4 + Z_8Z_2$$



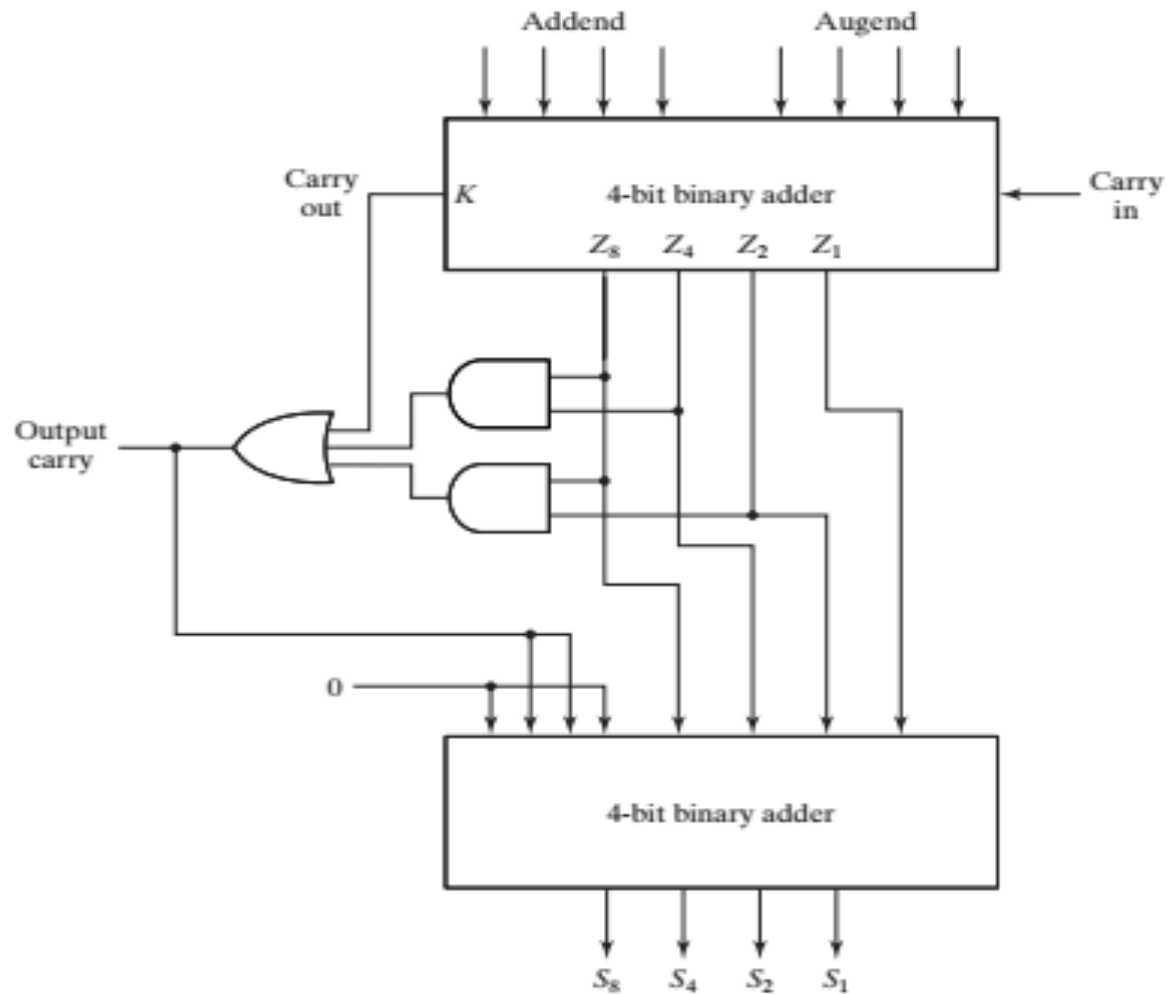

Block diagram of a BCD adder

Magnitude Comparator

- A *magnitude comparator* is a combinational circuit that compares two numbers A and B and determines their relative magnitudes.
- The outcome of the comparison is specified by three binary variables that indicate whether $A > B$, $A = B$ or $A < B$.
- Consider two numbers, A and B , with four digits each. Write the coefficients of the numbers in descending order of significance: $A = A_3 A_2 A_1 A_0$

$$B = B_3 B_2 B_1 B_0$$



The two numbers are **equal** if all pairs of significant digits are equal: $A_3=B_3, A_2=B_2, A_1=B_1$ and $A_0=B_0$

$$x_i = A_i B_i + A'_i B'_i \quad \text{for } i = 0, 1, 2, 3$$

The binary variable $(A = B)$ is equal to 1 only if all pairs of digits of the two numbers are equal.

$$(A = B) = x_3 x_2 x_1 x_0$$




To determine whether A is greater or less than B , we inspect the relative magnitudes of pairs of significant digits, starting from the most significant position.

$$(A > B) = A_3B'_3 + x_3A_2B'_2 + x_3x_2A_1B'_1 + x_3x_2x_1A_0B'_0$$

$$(A < B) = A'_3B_3 + x_3A'_2B_2 + x_3x_2A'_1B_1 + x_3x_2x_1A'_0B_0$$

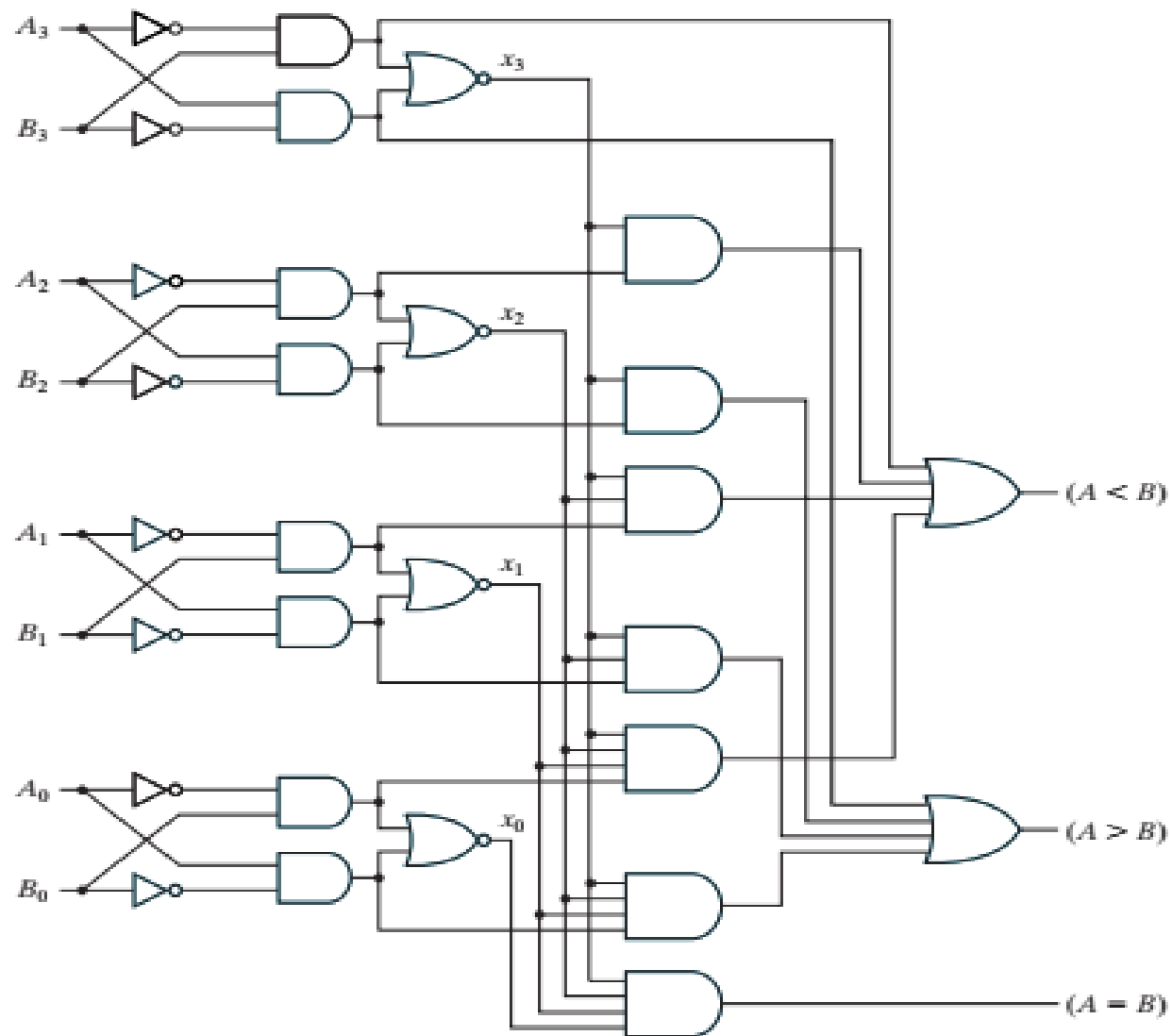The symbols $A > B$ and $A < B$ are binary output variables that are equal to 1 when $A > B$ and $A < B$, respectively.





Four-bit magnitude comparator



Example

Design a combinational circuit that compares two 4-bit numbers to check if they are equal. The circuit output is equal to 1 if the two numbers are equal and 0 otherwise.

$$x_i = A_i B_i + A_i' B_i' \quad \text{for } i = 0, 1, 2, 3$$

$$(A = B) = x_3 x_2 x_1 x_0$$



HDL for 4 bits Magnitude Comparator

// Dataflow description of a four-bit comparator

```
module mag_compare
```

```
( output  A_lt_B, A_eq_B, A_gt_B,
```

```
  input [3:0] A, B);
```

```
  assign A_lt_B = (A < B);
```

```
  assign A_gt_B = (A > B);
```

```
assign A_eq_B = (A == B);
```

```
endmodule
```



THANK YOU

