

DIGITAL LOGIC DESIGN LAB (EET1211)

LAB V: DESIGN AND TEST VARIOUS CODE CONVERTER CIRCUITS

Siksha 'O' Anusandhan Deemed to be University, Bhubaneswar

Branch: CSE		Section: M	
S. No.	Name	Registration No.	Signature
1.	BISWARANJAN SAHOO	2141019075	Biswaranjan Sahoo

Marks: ____/10

Remarks:

Teacher's Signature

I. OBJECTIVE:

1. Design a combinational circuit with four input lines that represent a decimal digit in BCD and four output lines that generate the 9's complement of the input digit.
2. Design a combinational circuit with four inputs and four outputs that converts a 4bit binary number into the equivalent 4bit Gray code.
3. Design a combinational circuit that accepts a 2-bit number and generate output binary number equal to the square of the input number.

II. PRE-LAB

For Obj. 1:

- a. Write the truth table for the circuit.
- b. Derive the Minimized Boolean expression for each output of the circuit.
- c. Draw the logic diagram for the circuit.
- d. Write HDL code.

For Obj. 2:

- a. Write the truth table for the circuit.
- b. Derive the Minimized Boolean expression for each output of the circuit.
- c. Draw the logic diagram for the circuit.
- d. Write HDL code.

For Obj. 3:

- a. Write the truth table for the circuit.
- b. Derive the Minimized Boolean expression for each output of the circuit.
- c. Draw the logic diagram for the circuit.
- d. Write HDL code.

OBJECTIVE-1

a)

	A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	0	0	1
1	0	0	0	1	1	0	0	0
2	0	0	1	0	0	1	1	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	0	1
5	0	1	0	1	0	1	0	0
6	0	1	1	0	0	0	1	1
7	0	1	1	1	0	0	1	0
8	1	0	0	0	0	0	0	1
9	1	0	0	1	0	0	0	0
10	1	0	1	0	0	0	0	0
11	1	0	1	1	0	0	0	0
12	1	1	0	0	0	0	0	0
13	1	1	0	1	0	0	0	0
14	1	1	1	0	0	0	0	0
15	1	1	1	1	0	0	0	0

[10-15 are unused bit. They are considered as don't care conditⁿ]

$$W = \sum m(0, 1)$$

b)

AB \ CD	00	01	11	10
00	1	1		
01				
11	X	X	X	X
10			X	X

$$W = A'B'C'$$

AB \ CD	00	01	11	10
00			1	1
01	1	1		
11	X	X	X	X
10			X	X

$$X = B \oplus C$$

AB \ CD	00	01	11	10
00			1	1
01			1	1
11	X	X	X	X
10			X	X

$$Y = C$$

AB \ CD	00	01	11	10
00	1			1
01	1			1
11	X	X	X	X
10	1		X	X

$$Z = D'$$



OBJECTIVE - 2

a)

B_3	B_2	B_1	B_0	G_3	G_2	G_1	G_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	0	1
1	1	1	0	1	0	0	0

b)

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00				
01				
11	1	1	1	1
10	1	1	1	1

$G_3 = B_3$

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00				
01	1	1	1	1
11				
10	1	1	1	1

$G_2 = B_2 \oplus B_3$


$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00			1	1
01	1	1		
11	1	1		
10			1	1

$G_1 = B_1 \oplus B_2$

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00		1		1
01		1		1
11		1		1
10		1		1

$G_0 = B_0 \oplus B_1$

c)

 

d) HDL Code

```

module obj2(B3, B2, B1, B0, G3, G2, G1, G0);
  output G3, G2, G1, G0;
  input B3, B2, B1, B0;
  assign G3 = B3;
  assign G2 = B2 & B3;
  assign G1 = B1 & B2;
  assign G0 = B0 & B1;
endmodule

```

d) HDL Code

```

module obj1(A, B, C, D, W, X, Y, Z);
  output W, X, Y, Z;
  input A, B, C, D;
  wire w1, w2, w3;
  assign w = (!A) & (!B) & (!C);
  assign X = B ^ C;
  assign Y = C;
  assign Z = (!D);
endmodule

```

OBJECTIVE-3

a)

A	B	W	X	Y	Z
0	0	0	0	0	0
0	1	0	0	0	1
1	0	0	1	0	0
1	1	1	0	0	1

b)

$$W = AB$$

$$X = A\bar{B}$$


$$Y = 0$$

$$Z = \bar{A}B + AB$$

$$= B(\bar{A} + A)$$

$$= B$$

c)

 

d) HDL Code

```
module obj3(A, B, W, X, Y, Z);  
  input A, B;  
  output W, X, Y, Z;  
  assign W = A & B;  
  assign X = A & !B;  
  assign Y = 0;  
  assign Z = B;  
endmodule.
```