

DIGITAL LOGIC DESIGN LAB (EET1211)

LAB VIII: CONSTRUCT, TEST AND INVESTIGATE THE OPERATION OF VARIOUS SHIFT REGISTER CIRCUITS

Siksha 'O' Anusandhan Deemed to be University, Bhubaneswar

Branch:		Section:	
S. No.	Name	Registration No.	Signature

Marks: _____/10

Remarks:

Teacher's Signature

I. OBJECTIVE

1. Design and Test of 4-bit SISO(Serial in Serial out) shift register
2. Design and Test of 4-bit SIPO (Serial in Parallel out) shift register
3. Design and Test of 3-bit PISO (Parallel in Serial out) shift register
4. Design and Test of 4-bit PIPO (Parallel in Parallel out) shift register

II. PRE-LAB

For Obj. 1:

- a. Draw the logic diagram for 4-bit SISO shift register.
- b. Write HDL code for 4-bit SISO shift register.

For Obj. 2:

- a. Draw the logic diagram for 4-bit SIPO shift register.
- b. Write HDL code for 4-bit SIPO shift register

For Obj. 3:

- a. Draw the logic diagram for 3-bit PISO shift register
- b. Write HDL code for 3-bit PISO shift register

For Obj. 4:

- a. Draw the logic diagram for 4-bit PIPO shift register
- b. Write HDL code for 4-bit PIPO shift register

III. LAB:

Components Required:

<u>S. No</u>	<u>Name of the Component</u>	<u>Specification</u>	<u>Quantity</u>
--------------	------------------------------	----------------------	-----------------

HDL Program:

Observation:

Conclusion:

IV. POST LAB

1. The bit sequence 0010 is serially entered (right-most bit first) into a 4-bit parallel out shift register that is initially clear. What are the Q outputs after two clock pulses?
 - A. 0000
 - B. 0010
 - C. 1000
 - D. 1111
2. A bidirectional 4-bit shift register is storing the nibble 1101. Its **RIGHT/LEFT** input is HIGH. The nibble 1011 is waiting to be entered on the serial data-input line. After three clock pulses, the shift register is storing _____.
 - A. 1101
 - B. 0111
 - C. 0001
 - D. 1110
3. Assume that a 4-bit serial in/serial out shift register is initially clear. We wish to store the nibble 1100. What will be the 4-bit pattern after the second clock pulse? (Right-most bit first)
 - A. 1100
 - B. 0011
 - C. 0000
 - D. 1111